

## Logic Design (Part 4) Latches – Storage devices (Chapter 3 + Notes)

- Log in to a Windows laptop
- Download CedarLogic-Circuits-Latches.cdl file  
from webpage to your desktop and open in CedarLogic

Based on slides © McGraw-Hill  
Additional material © 2013 Farmer  
Additional material © 2021 Narahari


1

### Recap: Combinational Logic & Devices

- Basic logic gates (AND, OR, NOT,....)
  - Built using transistors
- Combinational (more complex) logic devices
  - Multiplexers, Decoders, Adders, Sub, Multipliers, Comparators ( $x=y?$ )
  - Behavior modeled using a Boolean function
  - Built using logic gates
- Our current "library": basic logic gates, combinational logic devices
  - To build a circuit we can use anything from the library....
  - Is this enough?

2

## So Far: Combinational Logic

 

- Combinational Logic:
  - Always gives the same output for a given set of inputs
  - Aka “state-less” (i.e., no “state” or “memory”)
- Sequential Logic:
  - Its output depends on its inputs & its last output!
  - Forms the basis for “state” or “memory” for a computer

3


## Next . . Circuits with “memory”

- First we need to build a device that can store a bit
  - Using our current ‘library’ of gates
  - Building memory follows
- How to model sequential circuits/machines
  - Methodology for designing these machines: **Finite state machine**
  - Model as a directed graph
- How do we “synchronize” and “coordinate” the different pieces in the circuit....enter the CLOCK
- can we use a sequential circuit to “control” how computations take place in a processor ?
- Is a sequential circuit = Computer ?
  - Limitations of sequential machines..more in Foundations course

4
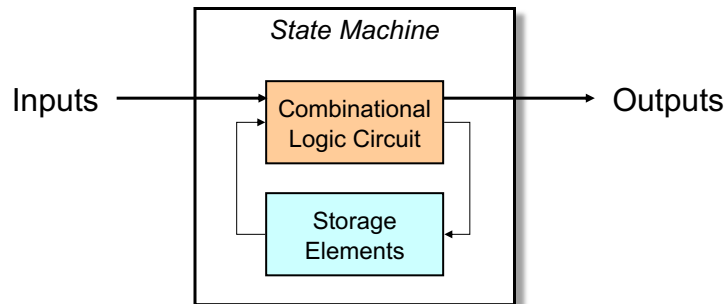
## (Finite) State Machine

- type of sequential circuit
  - Combines combinational logic with **storage**
  - “Remembers” state, and changes output (and state) based on **inputs** and **current state**



5

## Sequential Logic: Starting point

- Where do we start: Build a device, using combinational logic devices, to **store** a value
  - RS Latch
    - Use this to build a more useful/easier to use latch – the D Latch
  - concept of memory
- Build it using the devices we have thus far
  - How ? Use “feedback” circuit


6

## Feedback Circuits

- What happens if we feed the output of a combinational logic circuit to an input in the circuit ?
  - This is the key to circuits that can store values!

- Stable circuit

 - Output point of circuit retains value indefinitely
- If Q=1 it will remain 1
- If Q=0 it will remain 0



- Unstable circuit

- State that remains constant only for a duration of a few gate delays

- key takeaway: build stable circuits that can “hold” their value

7


## Latches and Flip-Flops

- Latch: basic circuit for storage
  - Operate on changes in Level (i.e., 1 or 0)
- Flip-flop:
  - Sequential circuits take input from output of storage
  - Latches that work on change of level can lead to unstable sequential circuits
    - As level changes the outputs change --- inputs change!
  - Flip-Flop circuits designed to operate properly when they are part of a sequential circuit
  - Designed to work in a synchronized circuit with a **Clock**

8
 
## R-S Latch


- The R-S latch is a bi-stable circuit which means that it can happily exist in either of two stable states. Just like a see-saw.
- You can push the latch from one state to another by setting or resetting it with the S-R signals
- The logic levels are maintained because of the feedback paths from outputs to inputs.



9
 
## Most Basic Sequential Logic Circuit: R-S Latch

- Most fundamental unit for static memory
  - Has the ability to “store” its last output
- R-S Latch – Cross-Coupled NAND gates
  - Output of each NAND gate serves as input to the other
  - Two inputs: **S** (*SET*) & **R** (*RESET*)
  - Two outputs: **Q** and **NOT(Q)** Recall:  $\text{NOT}(Q) = \sim Q = Q' = \bar{Q}$
  - Called a “Latch” because it can “Latch” onto data coming in



10


## R-S Latch – Behavior/Truth Table

- First, recall truth table for a NAND gate:

A	B	C
0	0	1
0	1	1
1	0	1
1	1	0

- R-S Latch Operation:

- Best place to start is  $S=1, R=0$

 

Next, look at top NAND gate

→ Its inputs are: 1 and 1

Blue 1, comes from lower NAND

→ Produces a 0 at its output

Therefore, when  $S=1, R=0$

The output of latch is:  $Q=0, \sim Q=1$


11

## Most Basic Sequential Logic Circuit: R-S Latch

- First, recall truth table for a NAND gate:

A	B	C
0	0	1
0	1	1
1	0	1
1	1	0

- R-S Latch Operation:

 

Truth Table for R-S Latch:

ACTION	S	R	Q	$\sim Q$
	0	0		
	0	1		
RESET	1	0	0	1
	1	1		

Called the “RESET” action, as Q is set to 0  
Also, notice: Q and  $\sim Q$  opposite

12


## Most Basic Sequential Logic Circuit: R-S Latch

- Truth table for a NAND gate:

A	B	C
0	0	1
0	1	1
1	0	1
1	1	0

Next, set S=1 R=1  
Check value of Q

- R-S Latch Operation:

 

Truth Table for R-S Latch:

ACTION	S	R	Q	~Q
	0	0		
SET	0	1	?	?
RESET	1	0	0	1
	-	-	-	-
HOLD	1	1	0	1

HOLD's last value on its outputs!

OUTPUT depends on input and last output

13

## Most Basic Sequential Logic Circuit: R-S Latch


- Truth table for a NAND gate:

A	B	C
0	0	1
0	1	1
1	0	1
1	1	0

Next, set S=0 R=1  
Check value of Q

- R-S Latch Operation:

 - Next input case is called the "SET", when inputs are: S=0, R=1



1<sup>st</sup> look at upper NAND gate  
→ Its inputs are: 0 and X (anything)  
→ Produces a 1 at its output  
Lower NAND gate  
→ Inputs are: 1 and 1  
→ Produces a 0 at its output


14

## Most Basic Sequential Logic Circuit: R-S Latch

- Truth table for a NAND gate:

A	B	C
0	0	1
0	1	1
1	0	1
1	1	0

- R-S Latch Operation:

 

Truth Table for R-S Latch:

ACTION	S	R	Q	$\sim Q$
	0	0		
SET	0	1	1	0
RESET	1	0	0	1
	1	1		

SETs LATCH to have a "1" at the output

15

## Most Basic Sequential Logic Circuit: R-S Latch


- Truth table for a NAND gate:

A	B	C
0	0	1
0	1	1
1	0	1
1	1	0

- R-S Latch Operation:

- Last valid input case is the "HOLD"  $S=1$ ,  $R=1$

 - If we have just "SET" Latch, we will have  $Q=1$ ,  $\sim Q=0$ , already on outputs



Upper NAND gate

→ Has  $S=1$  & former value of  $\sim Q=0$

→ Produces a 1 at its output

(same  $\sim Q$  as when it started)

Lower NAND gate

→ Inputs are: 1 and 1

→ Produces a 0 at its output (same Q)

16




## Most Basic Sequential Logic Circuit: R-S Latch

- Truth table for a NAND gate:

A	B	C
0	0	1
0	1	1
1	0	1
1	1	0

Next, set S=1 R=1  
Check value of Q

- R-S Latch Operation:

 


Truth Table for R-S Latch:

ACTION	S	R	Q	~Q
	0	0		
SET	0	1	1	0
RESET	1	0	0	1
HOLD	1	1	1	0

HOLD's value we "SET" last

17
 
## Storage - Cross-Coupled NANDs (R-S Latch)



- Set value of Q by R=0 or S=0
- Store value of Q with R=1, S=1
- What happens with S=0 and R=0?
  - Short answer: confusion
  - Real circuits depend on both Q and ~Q
  - Strange things may happen if both are 1

ACTION	S	R	Q	~Q
ILLEGAL	0	0	1	1
SET	0	1	1	0
RESET	1	0	0	1
HOLD	1	1	1	0
HOLD	1	1	0	1

D-Latches shows a way to prevent  
the RS Latch from ever getting S=R=0 as its input

18


## Circuits with Memory

- We now have a device (RS Latch) that is capable of storing a bit
  - It hold the previous value of Q
- but need to make sure the inputs are never  $R=S=0$
- Modify the circuit to get a D latch

19
 
## Gated D-Latch: Preventing “Illegal State” of RS Latch


- Add logic to an R-S latch
  - Create a more convenient interface (1) prevent  $S=0 \ \&\& \ R=0$  and (2) control when you can “write” into storage
- Two inputs: D (data) and WE (write enable)
  - When  $WE = 1$ , latch is set to value of D
    - $S = \text{NOT}(D), R = D$



20
 
## Gated D-Latch: Preventing “Illegal State” of RS Latch


- Add logic to an R-S latch
  - Create a more convenient interface, prevent  $S=0$  &&  $R=0$
- Two inputs: D (data) and WE (write enable)
  - When  $WE = 1$ , latch is set to value of D
    - $S = \text{NOT}(D)$ ,  $R = D$
  - When  $WE = 0$ , latch continues to hold previous value
    - $S = R = 1$  (hold condition for SR latch)
  - Extra logic does not allow  $S=0$ ,  $R=0$  case to occur



21
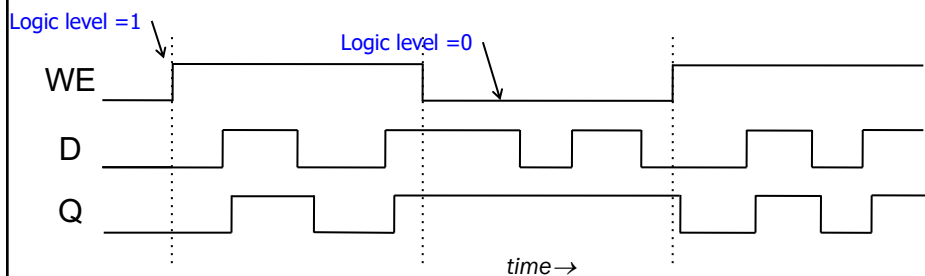
## D-Latch Timing Diagram


- The diagram below is called a “Timing” Diagram
  - Our D-Latch is previous-state dependent
    - We can think of this as a time dependency
    - Moving to the right on diagram, represents forward moving time
  - The inputs & outputs to our D-Latch are on left
    - Inputs/Outputs can be either “HIGH” (logic 1) or “LOW” (logic 0)
  - Think of this as a time-dependent truth table



22
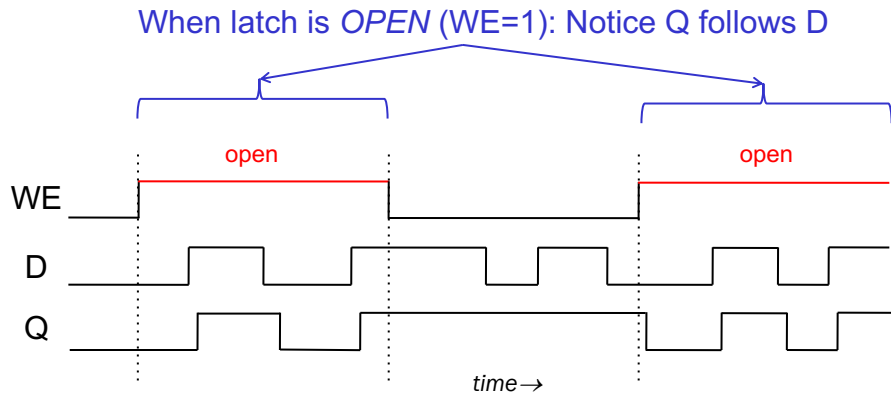
## D-Latch Timing Diagram


- When the WE signal is high the latch is said to be **open** and the output signal, Q, follows the input signal, D.
  - As in any combinational circuit there will be a small delay between the time that the input changes and the time that the output follows suit.



23
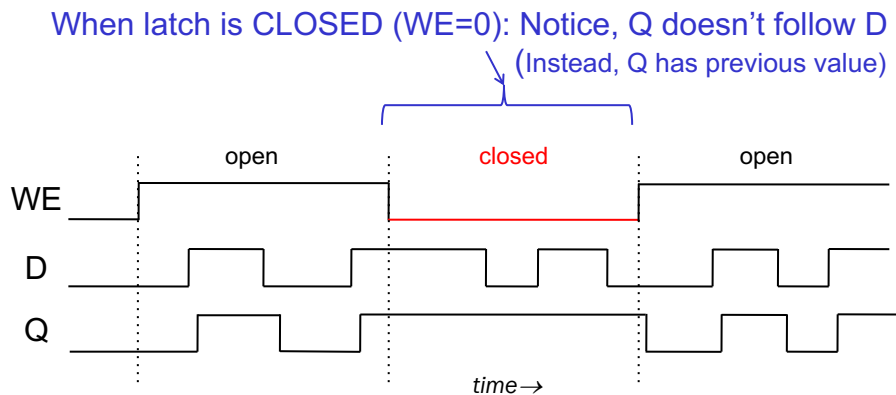
## D-Latch Timing Diagram


- When the WE signal is low the latch is **closed** and the output signal, Q, retains its value.



24
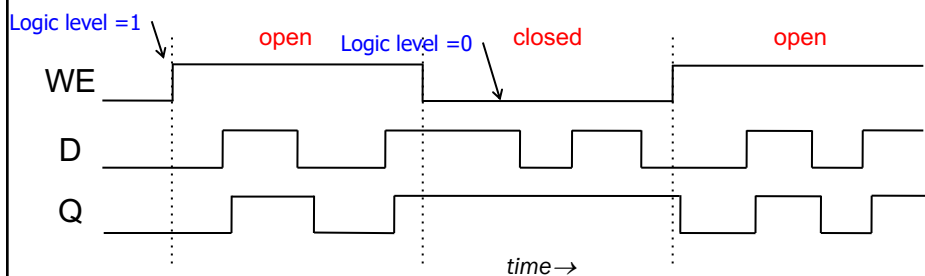
## D-Latch Timing Diagram


- Setup / Hold Times
  - The input signal should (D) be stable a certain amount of time before the WE signal is set to CLOSED (WE=0)
    - This is referred to as the **SETUP time**
  - In addition, the input signal (D) must be stable for a time after the WE is set to CLOSED (WE=0)
    - This is referred to as **HOLD time**
  - **Why?** Time must be given for inputs to propagate through NAND gates!  
Gates are not instantaneous!



25
 
## Next... Storage Devices

- we now have a device ( D-Latch) that can store a bit
  - Abstract the device: input D, WE; output/storage Q



- Use this to build 'real' storage devices....
- Temporary storage in a computer...**Register**
  - Where are variables stored before being sent to the arithmetic unit for operations on them?
  - Can we build an n-bit register using latches?
- What about "main" **memory**
  - Memory hierarchy ?

26


## Question: Page 4 of Latches.cdl file

- Describe behavior

27
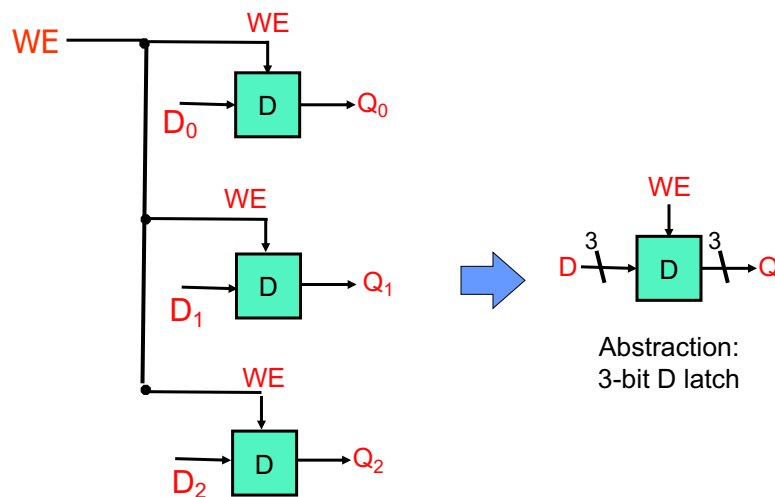
## Multi-Bit D-Latch: Register ?


- A collection of D-latches, controlled by a common WE
- When WE=1, 3-bit value D is written to the outputs



28

 
## Multi-Bit D-Latch – Register: Inside the latches

- A collection of D-latches, controlled by a common WE
- When WE=1, n-bit value D is written to the outputs



29

## A Basic Model of a Computer

 

Memory

CPU

Instructions

Essential Part of Computer!

Basic Components: Address: Looks up data  
 Note: both are in binary

30

## Memory

- We know how to store  $m$ -bit number in a register
- How about many  $m$ -bit numbers ?
  - Address space
- How to fetch a specific  $m$ -bit number?
  - addressing


31

## Memory

- Now that we know how to store bits, we can build a memory – a logical  $k$  by  $m$  array of stored bits

Address Space:  
number of locations  
(usually a power of 2)

$k = 2^n$   
locations

 

Addressability:  
number of bits per location  
(e.g., byte-addressable)

$m$  bits

32



## Memory: Address space and total size

A large number of addressable fixed size locations

### ▪ Address Space

$n$  bits allow the addressing of  $2^n$  memory locations.

- Example: 24 bits can address  $2^{24} = 16,777,216$  locations (i.e. 16M locations).
- If each location holds 1 byte (= 8 bits) then the memory is 16MB.
- If each location holds one word (32 bits = 4 bytes) then it is 64 MB.

- **Total size of memory** is number of locations multiplied by number of bits  $m$  at each location = **Address Space \* Addressability =  $2^n * m$**

33


## Memory - Addressability

- Computers are either **byte** or **word** addressable
  - - i.e. each memory location holds either 8 bits (1 byte), or a full standard word for that computer (16 bits for the LC-3, more typically 32 bits, though now many machines use 64 bit words).
- Normally, a whole word is written and read at a time:
  - If the computer is **word** addressable, this is simply a single address location.
  - If the computer is **byte** addressable, and uses a multi-byte word, then the word address is conventionally either that of its most significant byte (**big endian** machines) or of its least significant byte (**little endian** machines).

34
 
## Memory Interface


- There are two basic operations on a memory
  - Selecting one of the memory locations to **read** from
  - Selecting one of the memory locations to **write** to
- Interface signals
  - A: n-bit address lines to select/specify a location
  - D<sub>out</sub> : Contents of selected location during read (m bits)
  - D<sub>in</sub> : Value to be stored during write (m bits)
  - WE : If WE = 1 then write operation, WE = 0, read operation



35
 
## Memory

- Looking from the outside, what do we need?
- READ operation: Given address A of N bits, fetch contents at that address
  - From 2<sup>N</sup> locations we *select* one of them to be sent to the output
- WRITE: Given address A of N bits, write into exactly one of the 2<sup>N</sup> locations.



36

### Question: Page 5 of Latches.cdl file

- Describe behavior

37

### Question: Devices to construct Memory ?

- 1. Do you have a device to store a m-bit number ?
- 2. For READ: do you have a device that can send one out of  $2^N$  inputs (inputs are in the  $2^N$  latches) ?
- 3. For WRITE: do you have a device that can enable exactly one Write Enable (WE) in the  $2^N$  D-latches ?


38

## Question: Devices to construct Memory ?

- Memory is a  $2^N$  by  $m$  array:
  - $2^N$  rows – each row/location address specified using  $N$  bits
  - Each row has/stores  $m$ -bits
- 1. Do you have a device to store a  $m$ -bit number ?
  - How many of them do you need for the entire  $2^N$  by  $m$  memory ?
- 2. For READ: do you have a device that can send one out of  $2^N$  inputs (inputs are in the  $2^N$  latches/registers) ?
  - We have  $2^N$  'registers' each of  $m$  bits
  - Need to be able to send (read) contents from exactly one of these
- 3. For WRITE: do you have a device that can enable exactly one Write Enable (WE) in the  $2^N$  D-latches ?

39

## Example: $2^2$ by 3-bit memory

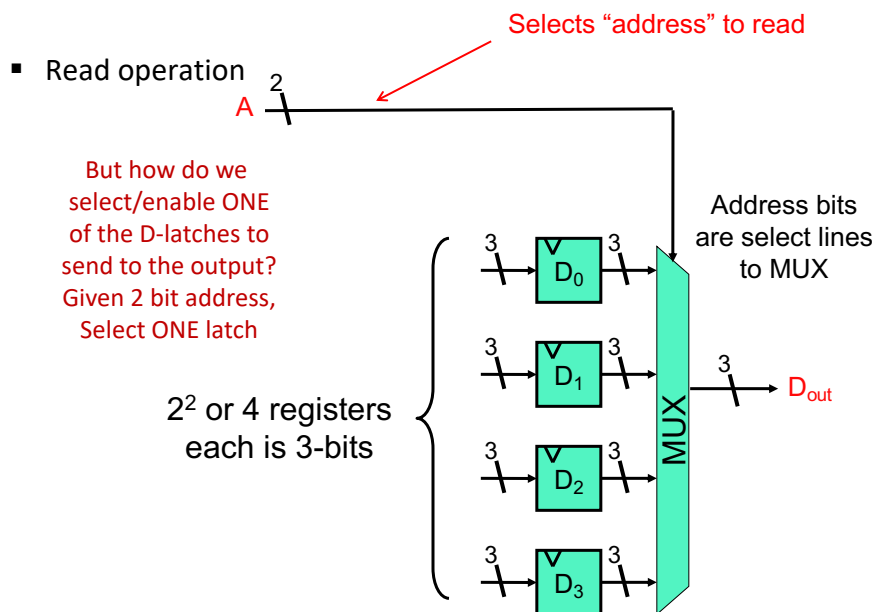

40


## Example: $2^2$ by 3-bit memory

How do we enable write into exactly one memory location

- Write operation

Use 2-4 Decoder:  
Input address bits = A,  
exactly one D-latch  
has WE=1

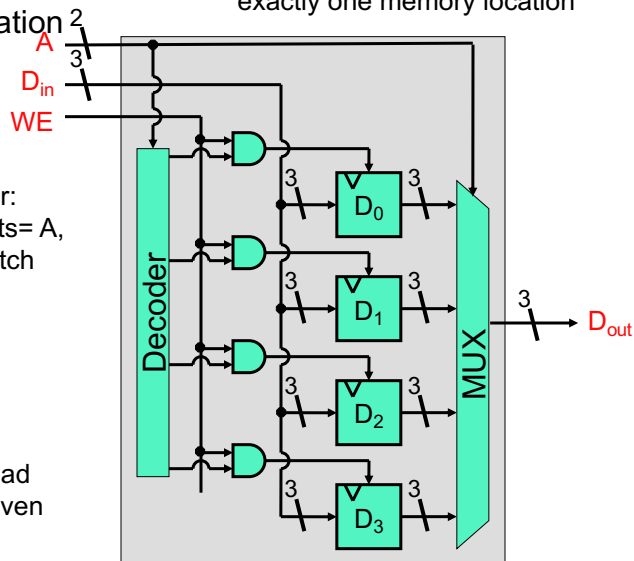*Limitation:*  
You can only read  
or write at any given  
time




41

## $2^2$ by 3-bit memory - Multiple "Ports"

- Independent Read/Write


You can read from one  
address  $A_R$  and write to  
another  $A_W$  with this  
arrangement

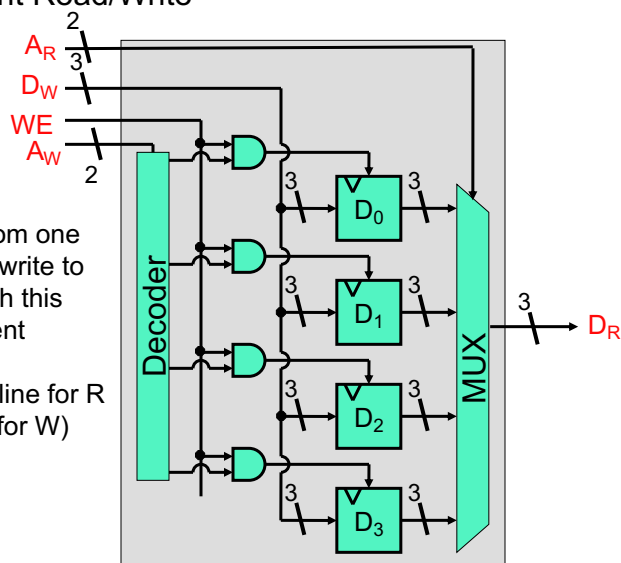(notice 1 address line for R  
1 address line for W)



42
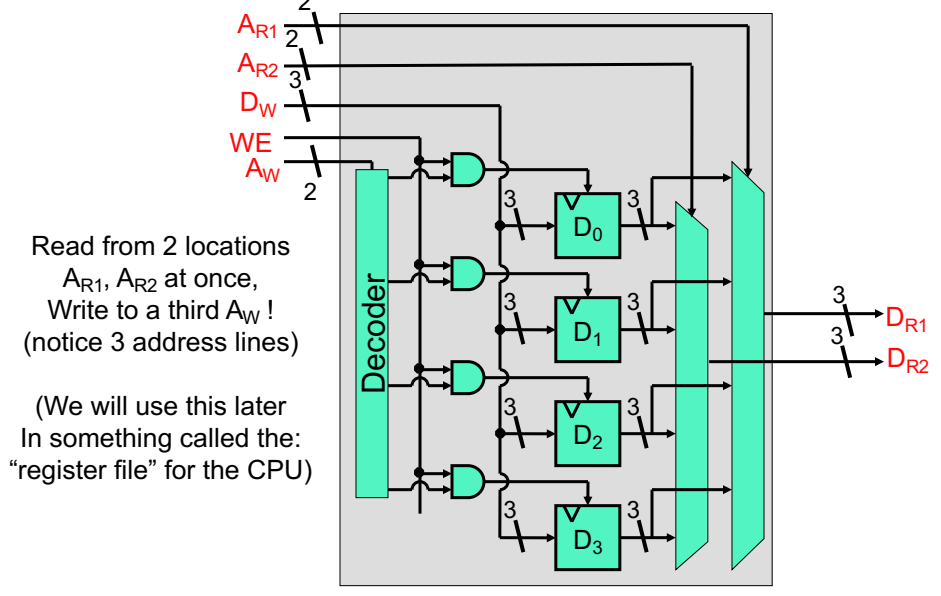
## 2<sup>2</sup> by 3-bit memory - Multiple Read Ports



43

## More Memory Details

- This is still not the way actual memory is implemented
  - Real memory: fewer transistors, denser, relies on analog properties
- But the logical structure is similar
  - Address decoder
  - Word select line, word write enable
  - Bit line
- Two basic kinds of **RAM** (Random Access Memory)
  - **Static RAM** (SRAM) - 6 transistors per bit
    - Fast, maintains data as long as power applied
  - **Dynamic RAM** (DRAM) - 1 transistor per bit
    - Denser but slower, relies on “capacitance” to store data, needs constant “refreshing” of data to hold charge on capacitor


*Also, non-volatile memories: ROM, PROM, flash, ...*

44
 
## Dynamic RAM

- Information stored as charge on capacitors.
- Capacitors leak so values have to be 'refreshed' continually
- As memory chips get larger, access times tend to increase. The processor spends more time waiting for data.

➤ This is a **major** issue limiting computer systems performance



45

## Speed mismatch: Example


- Intel Core i5 – Processor
  - Clock rates approx 2.5GHz, Clock period approx 0.4 ns
- DDR2-667 PC2-5300 SO-DIMM – 2 GB Memory
  - Can deliver at most 1 64-bit word every 1.5 ns
- Mismatch between processor speed and memory speed



46
 
## Memory Hierarchy

- Modern computers try to mitigate memory delays by exploiting locality of reference through caches.
- Smaller, faster memory stores are placed closer to the CPU and bulk transfers from slower memory are used



47

## Next: Design process for Sequential Circuits – Finite State Machines

- Recap: we now have a set of devices capable of storing bits
  - D-latch, Register, Memory (?),...
- Definition of sequential circuits
  - Components of a sequential circuit
- synchronization using a **CLOCK**
  - Modifying latches to work with a clock...Flip Flops
  - Flip Flops are the basic unit of storage in sequential circuits
- Designing sequential circuits – methodology ?
  - Finite state machine diagrams
  - Mapping to truth table.....build circuit

48



## Next: Design process for Sequential Circuits – Finite State Machines

- Definition of sequential circuits
  - Components of a sequential circuit
- synchronization using a **CLOCK**
  - Modifying latches to work with a clock...Flip Flops
  - Flip Flops are the basic unit of storage in sequential circuits
- Designing sequential circuits – methodology ?
  - Finite state machine diagrams
  - Mapping to truth table.....build circuit